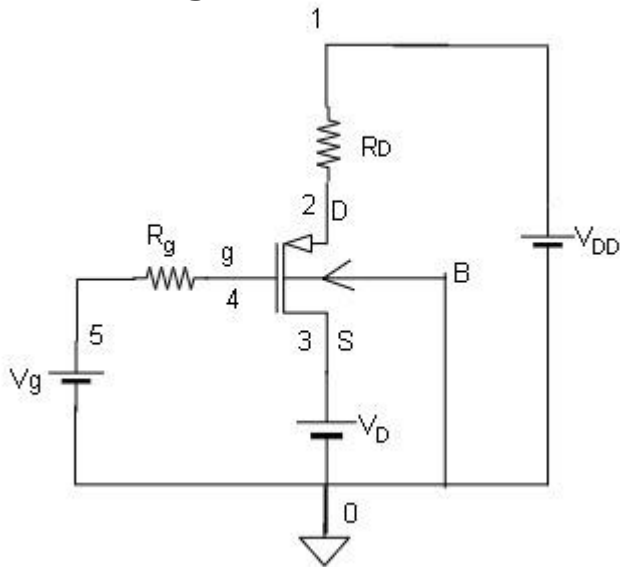


NMOS & PMOS CHARACTERISTICS USING SPICE


Aim: To plot the NMOS and PMOS Characteristics using SPICE.

Software required: Ubuntu 22.04, NGSPICE.

Circuit Diagrams:



(NMOS Characteristics)

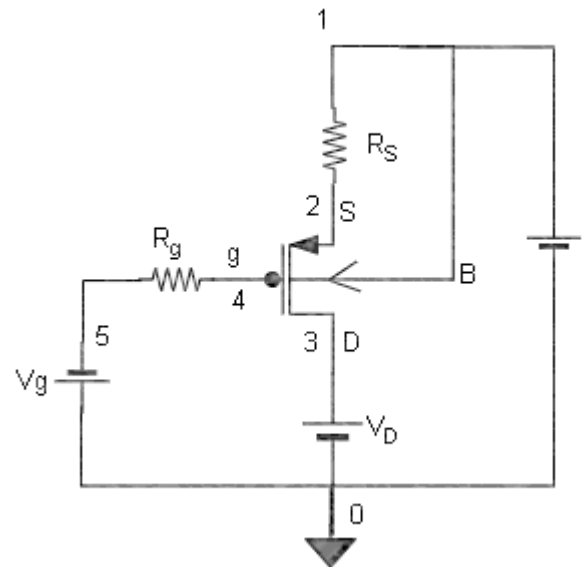

(PMOS Characteristics)

SPICE program for NMOS characteristics:

```


1 NMOS Characteristics
2
3 * Circuit parameters:
4 VDD      1 0 5
5 RD       1 2 100
6 VD       3 0 0
7 RG       4 5 100k
8 VG       5 0 5
9 M1       2 4 3 0 n_mos l=4u w=8u
10
11 * Defining model:
12 .model n_mos nmos(kp=20u vt0=0.7 lambda=0.01 gamma=0.02)
13
14 * DC analysis:
15 .control
16 dc VDD 0 5 0.1 VG 0 5 1
17 dc VG 0 5 0.1 VDD 0 5 1
18
19 * Plotting parameters:
20 set color0=rgb:f/f/b
21 set color1=rgb:0/0/0
22 set color2=rgb:f/0/0
23 set xbrushwidth=2
24
25 plot dc1.i(VD)
26 set color2=rgb:0/0/f
27 plot dc2.i(VD)
28
29 .endc
30 .end

```


SPICE program for PMOS characteristics:

```
1 PMOS Characteristics
2
3 * Circuit parameters:
4 VDD      1 0 5
5 VD       0 3 0
6 VG       5 0 -5
7 RD       1 2 100
8 RG       4 5 100k
9 M1       3 4 2 1 p_mos l=4u w=8u
10
11 * Defining model:
12 .model p_mos pmos(Vto=-0.7 Kp=20u lamda=0.3 Gamma=0.02)
13
14 * DC analysis:
15 .control
16 dc VDD 0 5 0.1 VG 0 -5 -1
17 dc VG 0 -5 -0.1 VDD 0 5 1
18
19 * Plotting parameters:
20 set color0=rgb:f/f/b
21 set color1=rgb:0/0/0
22 set color2=rgb:f/0/0
23 set xbrushwidth=2
24
25 plot dc1.i(VD)
26
27 set color2=rgb:0/0/f
28
29 plot dc2.i(VD)
30 .endc
31 .end
```

NMOS Characteristics

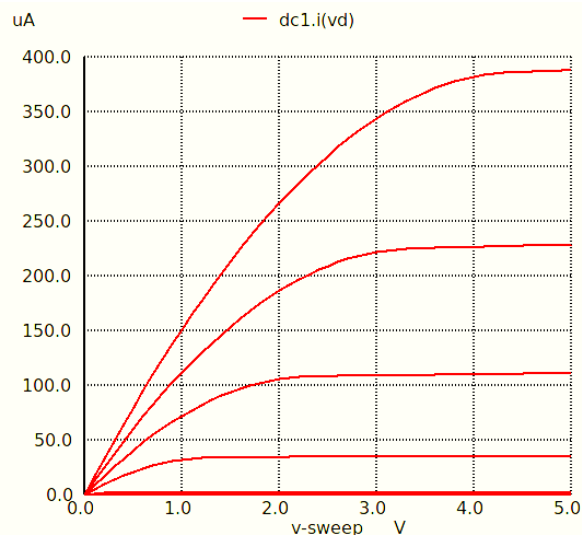


(I_D vs V_{DS} for NMOS)

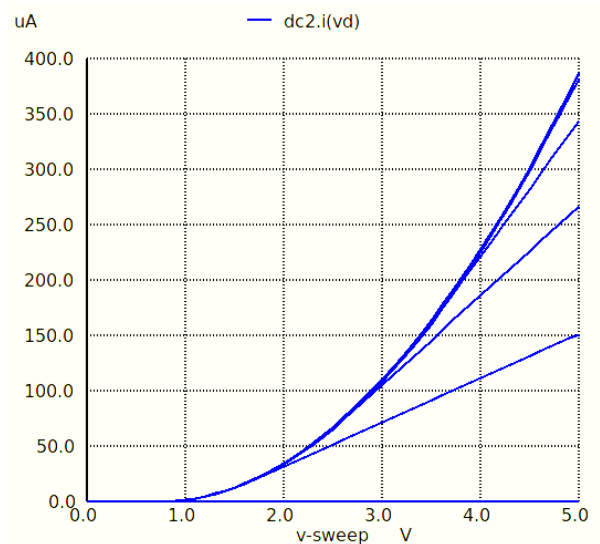


(I_D vs V_{GS} for NMOS)

PMOS Characteristics

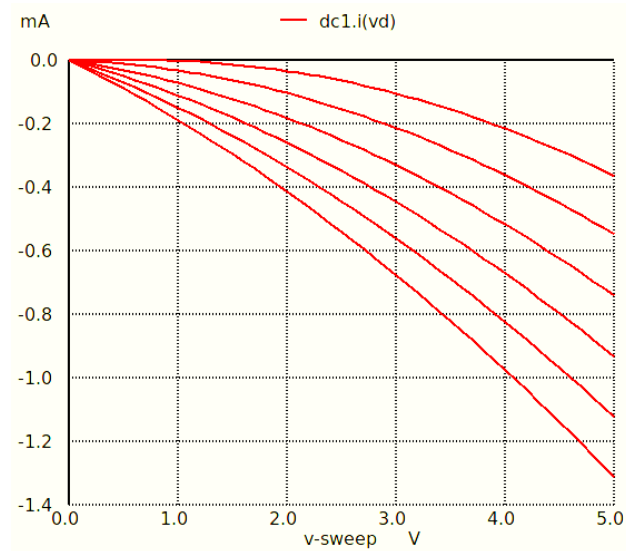

(I_D vs V_{DS} for PMOS)

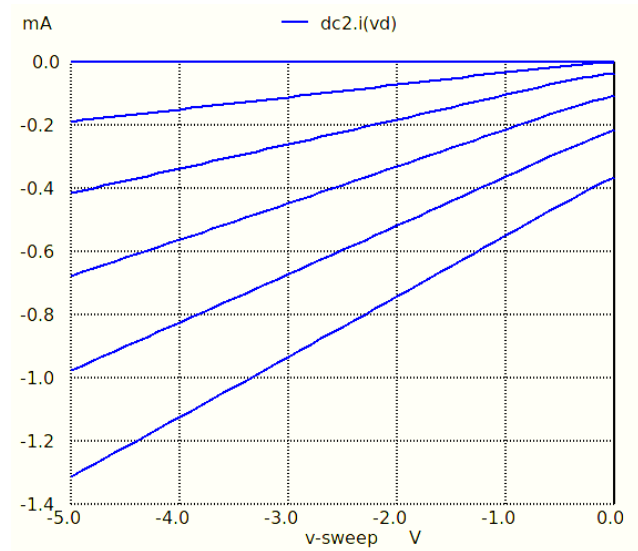

(I_D vs V_{GS} for PMOS)

Conclusion: The SPICE programs were written successfully to plot the PMOS and NMOS Characteristics.