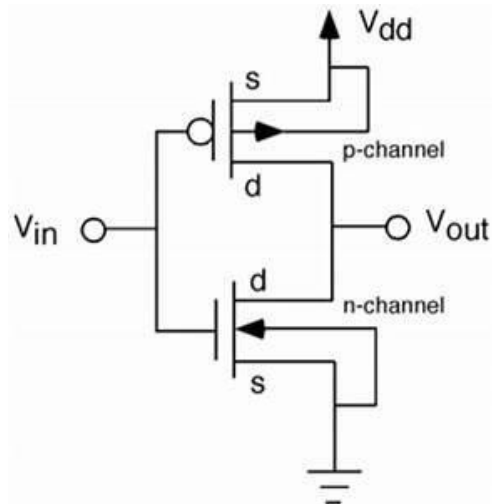



**AIM:** To draw the LAYOUT of CMOS Inverter in MAGIC, extract the parameters in SPICE and verify the functionality.

**SOFTWARE REQUIRED:** Ubuntu 10.1, NGSPICE, MAGIC

**DIAGRAM:**




**CMOS INVERTER Layout in MAGIC:**

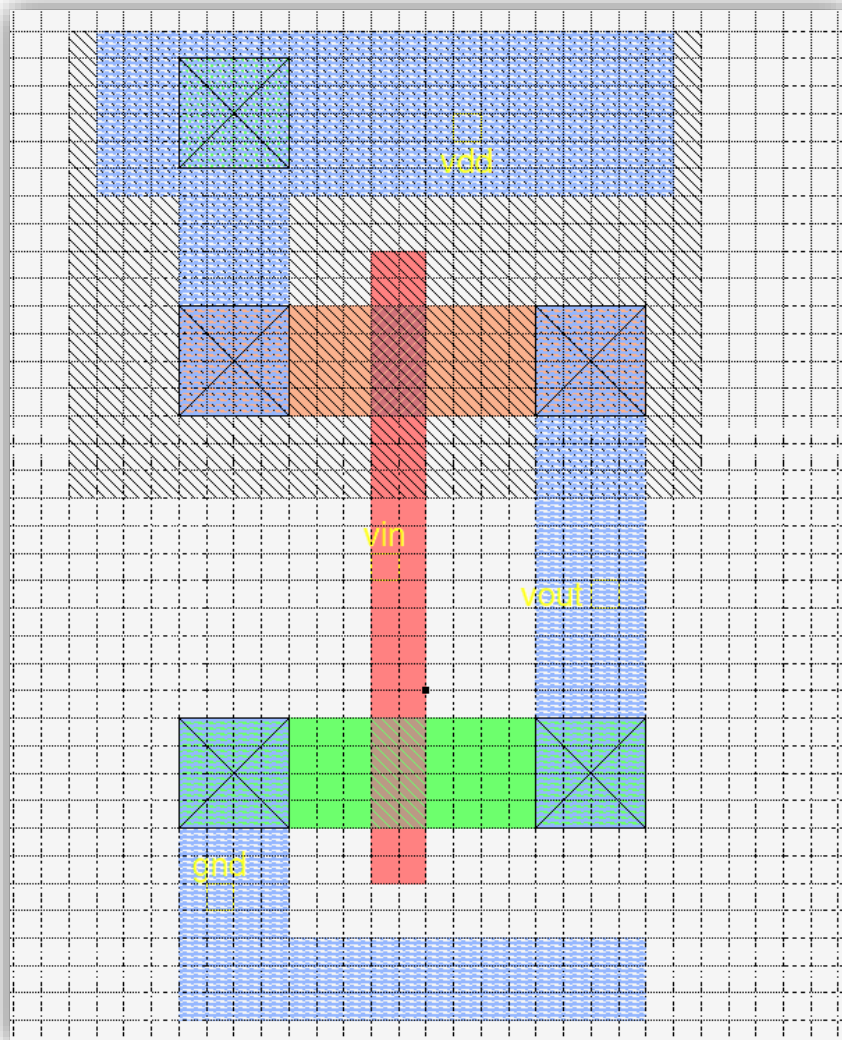

## SPICE CODE FOR CMOS INVERTER :

```
Open  aca.spice  Save  Ln 22, Col 1  INS
1 * SPICE3 file created from aca.ext - technology: scmos
2
3 .option scale=1u
4
5 M1000 Vout vin vdd vdd pfet w=4 l=2
6 + ad=32 pd=24 as=32 ps=24
7 M1001 Vout vin gnd gnd nfet w=4 l=2
8 + ad=32 pd=24 as=32 ps=24
9 C0 gnd gnd 4.89fF
10 C1 vin gnd 4.05fF
11
12 Vsupply vdd 0 5
13 vin1 vin 0 5
14 Vdummy gnd! 0 0
15 .model nfet nmos(kn=20u vto=0.7 lambda=0.01 gamma=0.001)
16 .model pfet pmos(kp=20u vto=-0.7 lambda=0.01 gamma=0.001)
17 .dc vin1 0 5 0.1
18 .control
19 run
20 plot v(Vout)
21 .endc
22 .end
```
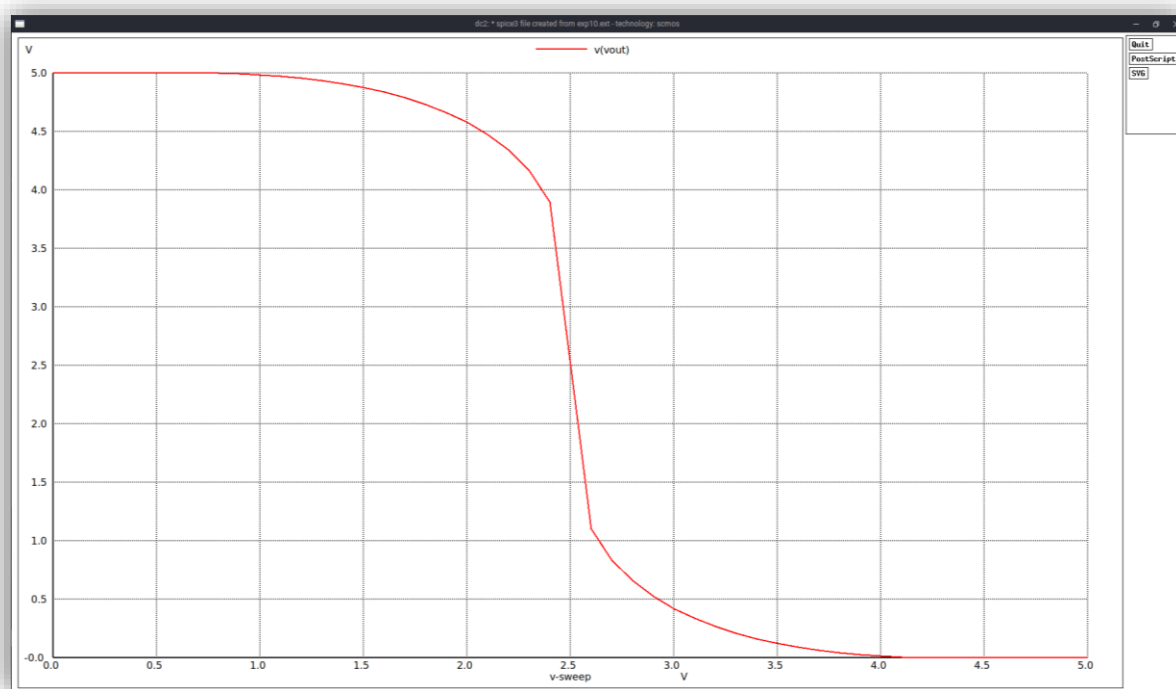
## OUTPUT: CMOS INVERTER CHARACTERISTICS :



**CONCLUSION:** The LAYOUT was successfully drawn, parameters extracted in SPICE and the characteristics of CMOS Inverter were verified.